

**University of Toronto**  
**Faculty of Applied Science and Engineering**

**ECE 360F - Introductory Electronics**

**Final Examination**

**December 2001**

**Examiner: Professor S. Zukotynski**

Name: \_\_\_\_\_

Student no: \_\_\_\_\_

Q	Max	Mark
1	25	
2	25	
3	25	
4	25	
Bonus	5	
Total	105	

Aid sheet allowed


Non-programmable calculator allowed

**ALL WORK TO BE MARKED IS TO BE DONE ON THESE SHEETS**

There are two spare pages at the back


## QUESTION 1 - OP-AMPS

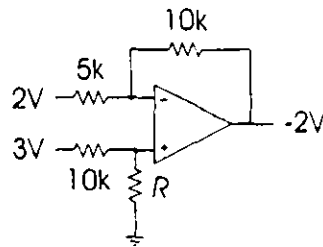Part A: The op-amp is ideal. Find  $R$  and the current in the feedback resistor. Show the current polarity on the figure.




$R =$   
 $I =$

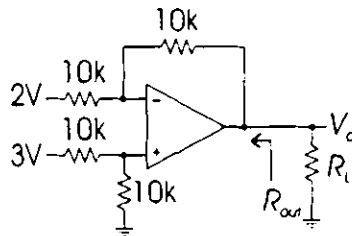Part B: The op-amp is ideal, except the open loop gain is 80dB and the output resistance is  $75\Omega$ . Find the output resistance of the amplifier circuit.





$R_{out} =$

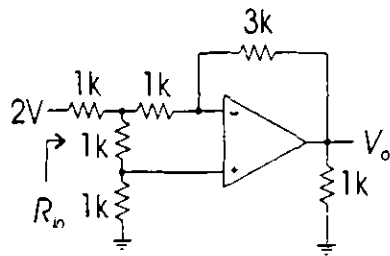Part C: The op-amp is ideal . Find  $R_{in}$  and  $V_o$





$R_{in} =$   
 $V_o =$

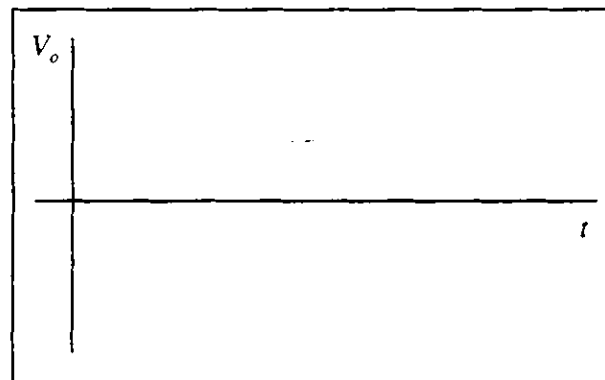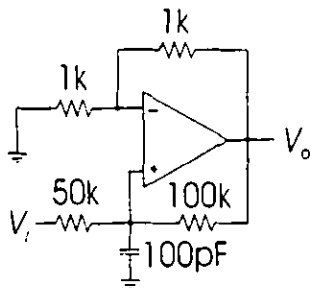Bonus: The op-amp is ideal.  $V_i$  is a square wave 2V peak-to-peak with a period of 2ms. Sketch one period of  $V_o$ . Clearly indicate the critical points, give their coordinates and give analytical expressions for the curves. Assume that negative feedback dominates positive feedback.




## QUESTION 2 - DIODES

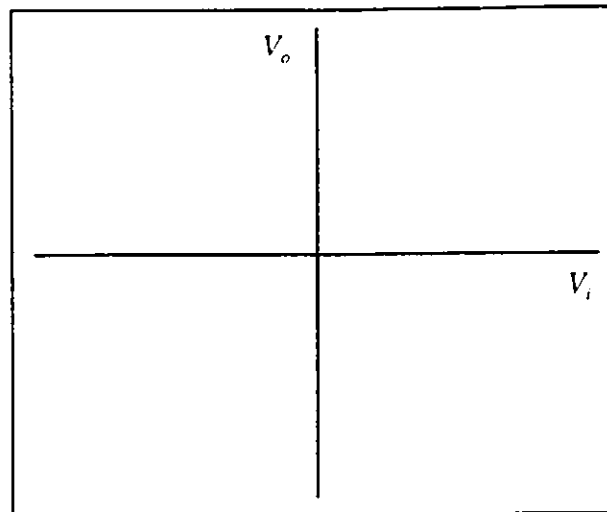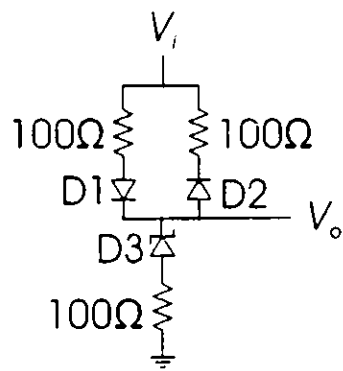Part A: All three diodes are ideal and  $V_Z=5V$  for D3. Sketch  $V_o$  for  $-10V \leq V_i \leq 10V$ . Indicate characteristic points and give their coordinates. Give the slope of the linear segments.



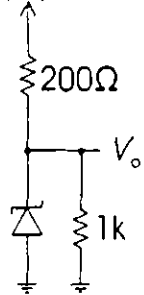Part B: The zener diodes has  $V_{ZT}=10V$  at  $I_{ZT}=100mA$  and  $r_z=4\Omega$ . Find  $V_o$  and the load and line regulation in the circuit.

$$V_i = [20 + 0.1 \sin(500 \text{ rad/s } t)] V$$





$V_o =$

Load regulation =

Line regulation =

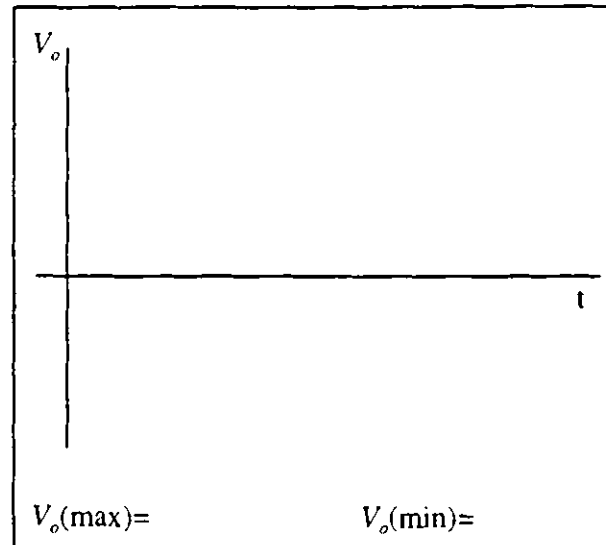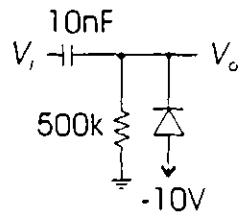
Part C: The diode is ideal. The square input voltage is 20V peak-to-peak with a period of 20ms. Sketch one period of  $V_o$ . Label the graph and give expressions for the curves (on the graph) and all of the critical values of  $V_o$ .



### QUESTION 3 - BJTs

Part A: For the three BJTs below,  $\beta=99$ . Find the emitter current and the voltages at the collector, base and emitter. Verify the mode of operation. Assume  $V_{CE(sat)}=0.2V$ .

i)

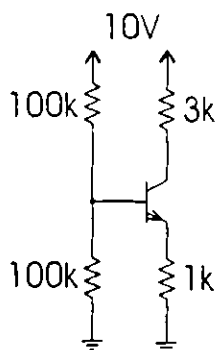

Mode of operation=saturation

$I_E=$


$V_C=$

$V_B=$

$V_E=$

Confirm mode of operation

ii)

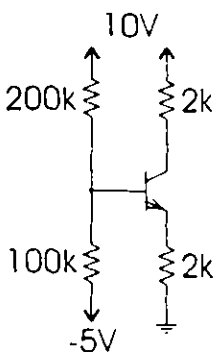

Mode of operation=cut off

$I_E=$


$V_C=$

$V_B=$

$V_E=$

Confirm mode of operation

iii)

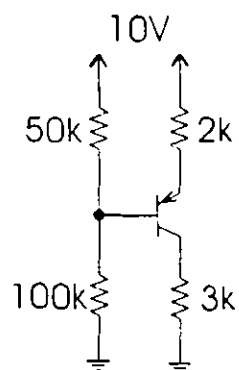

Mode of operation=active

$I_E=$


$V_C=$

$V_B=$

$V_E=$

Confirm mode of operation

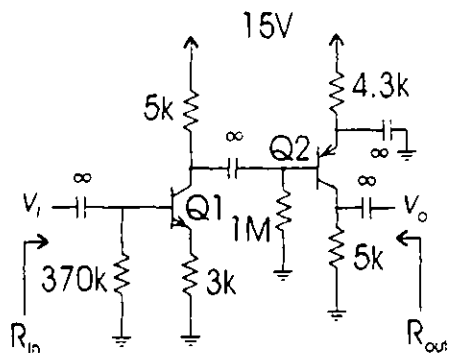Part B: Both BJTs have  $\beta=99$  and  $V_A=\infty$ . The dc emitter current of both transistors is 1mA. Replace Q1 with the T model and Q2 with the hybrid- $\pi$  model and sketch the equivalent amplifier circuit. Find the small signal  $R_{in}$ ,  $R_{out}$  and open circuit voltage gain  $A_{v0}$ . Assume  $V_T=25\text{mV}$ .



Equivalent small signal circuit

$$R_{in} =$$


$$R_{out} =$$

$$A_v =$$



#### QUESTION 4 - FETs

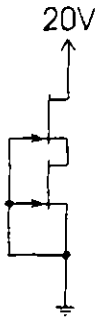Part A: The two JFET are identical with  $I_{DSS}=5\text{mA}$  and  $V_p=-2\text{V}$ . Assume  $\lambda=0$ . Find  $I_D$ .




$I_D =$

Part B: For the FET you have  $k=1\text{mA/V}^2$ ,  $V_t=2\text{V}$  and  $\lambda=1/100\text{V}$ . Assume  $V_i$  is small.

i) Show that the FET is in saturation.

The FET is in saturation because:

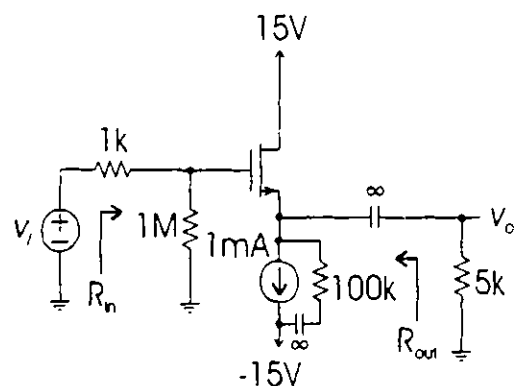

$g_m =$

ii) Calculate  $g_m$ , replace the transistor with its small signal model, sketch the amplifier circuit and give the value of all components.

b) Find  $R_{in}$ ,  $R_{out}$  and the small signal voltage gain  $V_o/V_i$ .

$R_{in} =$   
 $R_{out} =$   
 $V_o/V_i =$



