

University of Toronto

Department of Electrical and Computer Engineering

**ECE241- Digital Systems**

Final Examination

December 2001

TYPE A (No Aids)

Last Name: \_\_\_\_\_

First Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

Signature: \_\_\_\_\_

Duration: **2.5 hours**

**Answer ALL questions on this test paper.**

**There is extra space at the end if you need it.**

**EXAMINER's REPORT**

1	_____	/20
2	_____	/24
3	_____	/22
4	_____	/18
5	_____	/16
TOTAL	_____	/100

**Question 1 - [20 marks]**

1. Implement the following function by using exactly one 4-to-1 multiplexer, one NAND gate and one NOR gate.

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 4, 8)$$

**[4 marks]**

2. Implement the following function by using exactly one 4-to-1 multiplexer, one NAND gate and one NOR gate.

$$g(x_1, x_2, x_3, x_4) = \sum m(2, 3, 5, 7, 11, 13)$$


**[4 marks]**

3. Show how the following functions can be implemented using 3-input lookup tables (LUT).

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 4, 8)$$

$$g(x_1, x_2, x_3, x_4) = \sum m(2, 3, 5, 7, 11, 13)$$

 Use the **least number of LUTs** that you can. Draw the circuit containing the LUTs and indicate the function of each LUT by showing the logic function that it implements. For instance, if a LUT implements the function  $k = A\bar{B}C + AB\bar{C}$ , then you would draw the LUT in your circuit as shown below.



[Correct: 6 marks]

[Minimal: 6 marks]


## Question 2 – [20 marks]

A circuit has two inputs  $a$  and  $b$  and three outputs  $gt$ ,  $eq$  and  $lt$ . The outputs correspond to the results of the comparison between  $a$  and  $b$ . Each output is equal to 1 when the result of the comparison is true and 0 otherwise. This circuit could be called a “half comparator”.

$$gt = (a > b)$$

$$eq = (a = b)$$

$$lt = (a < b)$$

 

1. Give the expression for  $gt$ ,  $eq$  and  $lt$  by using AND, OR, NOT and XOR operators.

[3 marks]

ANSWER


$$gt =$$

$$eq =$$

$$lt =$$

 2. We now want to compare two 4-bit unsigned numbers  $A$  ( $a_3a_2a_1a_0$ ) and  $B$  ( $b_3b_2b_1b_0$ ) by using a “ripple comparator”. The basic block is the “1-bit comparator” which has five inputs  $a_i$ ,  $b_i$ ,  $gt_i$ ,  $eq_i$  and  $lt_i$  and three outputs  $gt_{i+1}$ ,  $eq_{i+1}$  and  $lt_{i+1}$ . It delivers the results of the comparison for stage  $i$  ( $gt_{i+1}$ ,  $eq_{i+1}$  and  $lt_{i+1}$ ) according to  $a_i$ ,  $b_i$  and the results of the comparisons for the previous stage ( $gt_i$ ,  $eq_i$  and  $lt_i$ ).

$gt$ ,  $eq$  and  $lt$  correspond respectively to greater than, equal; and less than.



Give the expressions for  $gt_{i+1}$ ,  $eq_{i+1}$  and  $lt_{i+1}$  by using AND, OR, NOT and XOR operators.

[3 marks]


ANSWER

$$gt_{i+1} =$$

$$eq_{i+1} =$$

$$lt_{i+1} =$$

 3. Design the corresponding circuits using NOT, NAND, XOR and XNOR gates. NAND gates can have any number of inputs. XOR and XNOR gates have two inputs. The output of a XNOR gate is 1 when the two inputs are equal; and 0 otherwise. The symbols for XOR and XNOR gates are shown below.



[4 marks]

ANSWER


The propagation delay of NOT and NAND gates is  $(p+1)/2$  ns, where  $p$  is the number of inputs. Not gate propagation delay is 1 ns. A 2-input NAND gate propagation delay is 1.5 ns, etc. The propagation delay of XNOR and XOR gates is 2 ns.

4. Fill out the following table which gives the propagation delay between the inputs and the output for the 1-bit comparator

[3 marks]

INPUT	TO	OUTPUT	Propagation delay (ns)
$a_i$ or $b_i$ (worst case)		$gt_{i+1}$	
$a_i$ or $b_i$ (worst case)		$eq_{i+1}$	
$a_i$ or $b_i$ (worst case)		$lt_{i+1}$	
$gt_i$		$gt_{i+1}$	
$eq_i$		$eq_{i+1}$	
$lt_i$		$lt_{i+1}$	

 
5. What is the worst case propagation delay for the 4-bit ripple comparator between the inputs and the final results of the comparison ( $gt_4$ ,  $eq_4$  and  $lt_4$ )? The scheme of the 4-bit ripple comparator is shown below



ANSWER (Show what is the critical path in the 4-bit comparator and give the value of the propagation delay in ns)

[4 marks]

 We now use the “look-ahead” technique to implement the 4 bit comparator (shown below)



6. Give the expressions of  $gt_4$ ,  $eq_4$  and  $lt_4$  for the 4-bit look-ahead comparator.

[3 marks]

$gt_4 =$

$eq_4 =$

$lt_4 =$

7. What is the worst case propagation delay using the same assumptions as for the ripple comparator?


**ANSWER (Show what is the critical path in the 4-bit comparator and give the value of the propagation delay in ns)**

[4 marks]
 
### Question 3 - [22 marks]

1 Design a modulo-11 counter with an Enable input by using

- the 4-bit counter below, which has Enable and Synchronous Load inputs
- logic gates (you can use NOT, AND, OR, NAND, NOR gates with any number of inputs).



ANSWER

[4 marks]



2. Design a *modulo-12* counter with four D Flip-Flops.

Give the minimal sum of products expression for inputs  $D_3$ ,  $D_2$ ,  $D_1$  and  $D_0$  of the flip-flops (the flip-flop outputs are  $Q_3$ ,  $Q_2$ ,  $Q_1$  and  $Q_0$ ; where  $Q_3$  is the most significant and  $Q_0$  is the least-significant bit).

[Correct: 4 marks]

[Minimal: 2 marks]

ANSWER


$D_3 =$

$D_2 =$

$D_1 =$

$D_0 =$

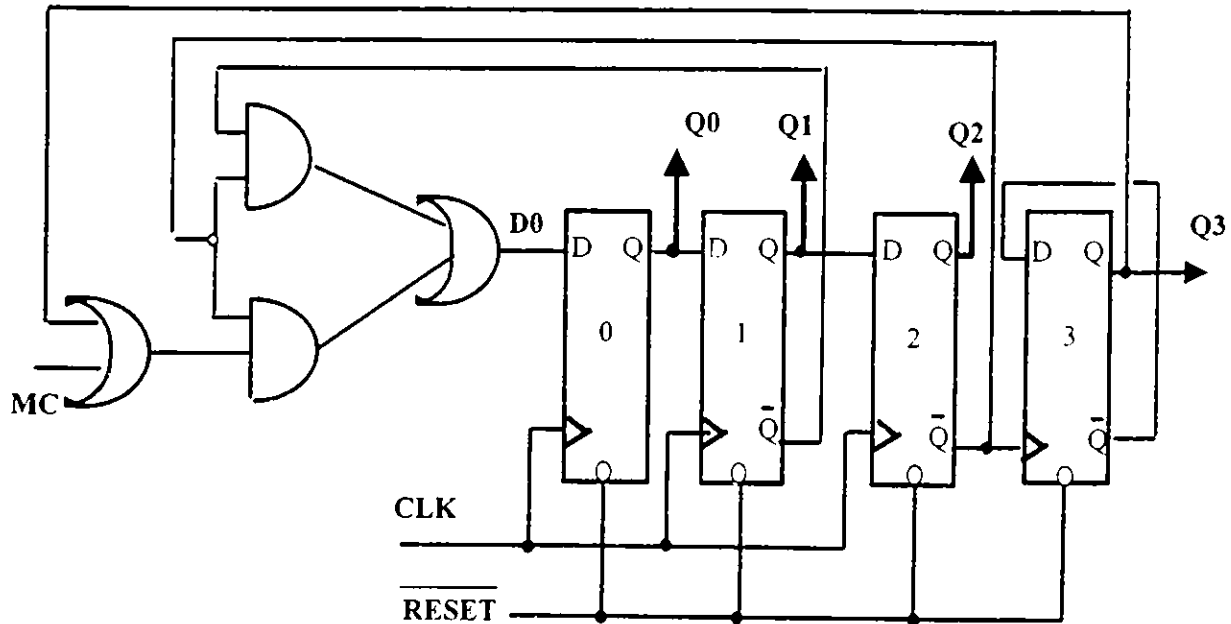3. The circuit below has 4 D Flip Flops, 1 input MC (Mode Count) and a clock CLK.



Give the sum of products expression for  $D_0$  as a function of the FF outputs when  $MC=0$  and when  $MC=1$ .

**ANSWER**

**[2 marks]**

**MC=0**

$$\mathbf{D}_0 =$$

MC=1

$$\mathbf{D}_0 =$$

4. Assume that all the FFs are initially reset by the asynchronous RESET signal.

What are the successive values of  $Q_0$   $Q_1$   $Q_2$   $Q_3$  after each clock cycle when  $MC=0$ ?

**ANSWER on the NEXT PAGE**

**[4 marks]**

5. All the FFs are again reset by the asynchronous RESET signal.

What are the successive values of  $Q_0$   $Q_1$   $Q_2$   $Q_3$  after each clock cycle when  $MC=1$ ?

**ANSWER on the NEXT PAGE**

**[4 marks]**



#### Question 4 - [18 marks]

A synchronous sequential circuit has two input lines,  $x_1$  and  $x_0$ , and two output lines,  $z_1$  and  $z_0$ . At each clock cycle, the combination  $x_1 x_0$  constitutes a 2-bit binary number ( $x_1$  is the most significant bit and  $x_0$  is the least significant bit). If the present value of the input number is less than the immediately preceding value, then the outputs are  $z_1 z_0 = 10$ . If the present value of the input number is greater than the immediately preceding values, then the outputs are  $z_1 z_0 = 01$ . If it is the same,  $z_1 z_0 = 00$ .

The FSM can be implemented as a Mealy machine with 2 D flip-flops.

1. Complete the state table below that corresponds to the Mealy implementation.

[8 marks]

PS	NS	NS	NS	NS	$z_1 z_0$	$z_1 z_0$	$z_1 z_0$	$z_1 z_0$
	$x_1 x_0$	$x_1 x_0$	$x_1 x_0$	$x_1 x_0$	$x_1 x_0$	$x_1 x_0$	$x_1 x_0$	$x_1 x_0$
$Q_1 Q_0$	00	01	11	10	00	01	11	10
00								
01								
11								
10								

2. Give the minimal sum of products expressions for the inputs of the D flip-flops and for the outputs.

ANSWER: (Use next page for rough work)

[Correct: 4 marks]

[Minimal: 4 marks]

$D_1$

$D_0$

$z_1$

$z_0$



### Question 5 - [20 marks]

The VHDL code given below is supposed to implement a finite state machine. It contains a significant mistake.

[5 marks]

1. Correct the mistake by giving the correct code in place of the wrong code.

#### CORRECT VERSION OF THE CODE

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fe2001 IS
    PORT ( Clock, Resetn, X : IN    STD_LOGIC ;
          Z : OUT STD_LOGIC ) ;
END fe2001;

ARCHITECTURE Behavior OF fe2001 IS
    TYPE State_type IS (A, B, C, D) ;
    SIGNAL state, next_state : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            state <= A ;
        ELSIF (Clock = '1') THEN
            state <= next_state ;
        END IF;
    END PROCESS ;

    PROCESS ( X, state )
    BEGIN
        CASE state IS
            WHEN A =>
                IF X='1' THEN
                    next_state <= B ;
                ELSE
                    next_state <= A ;
                END IF;
            WHEN B =>
                IF X='1' THEN
                    next_state <= C ;
                ELSE
                    next_state <= A ;
                END IF;
            WHEN C =>
                IF X='1' THEN
                    next_state <= C ;
                ELSE
                    next_state <= D ;
                END IF;
            WHEN D =>
                IF X='1' THEN
                    next_state <= B ;
                ELSE
                    next_state <= A ;
                END IF;
        END CASE;
    END PROCESS;
END Behavior;
```

```

                                END IF;
                        END CASE ;
                END PROCESS ;

        PROCESS ( X, state )
        BEGIN
                CASE state IS
                        WHEN A =>
                                Z <='0' ;
                        WHEN B =>
                                Z <='0' ;
                        WHEN C =>
                                Z <='0' ;
                        WHEN D =>
                                IF X='1' THEN
                                        Z <='1' ;
                                ELSE
                                        Z <='0' ;
                                END IF;
                        END CASE ;
                END PROCESS ;
        END Behavior ;

```

2. Draw the state diagram for the machine defined by this code.

**ANSWER**

**[6 marks]**

3. Is the FSM a Moore or a Mealy machine?

**ANSWER**

**[1 mark]**

4. What does the FSM do?

**ANSWER.**

**[4 marks]**

**EXTRA SPACE - USE ONLY IF NEEDED**



EXTRA SPACE - USE ONLY IF NEEDED

EXTRA SPACE - USE ONLY IF NEEDED