

University of Toronto
Dept. of Electrical and Computer Engineering
Final

Date - April 19, 2001

Duration: 2.5 Hr.

ECE231S — Introductory Electronics
Lecturers - D.A. Johns, N. Kherani, T. Koteski

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

1. Two handwritten aid-sheets allowed and calculator type unrestricted.
 2. Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.
-

Last Name: _____



First Name: _____

Student #: _____

Question	Mark
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
Total	


(max grade = 50)

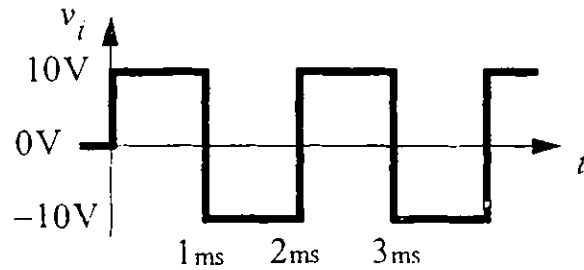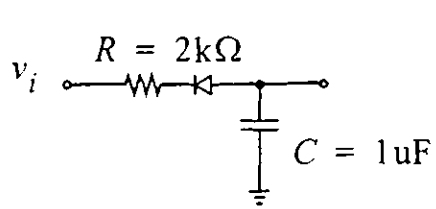- [5] **Question 1:** Consider the circuit below. Assuming the diode is ideal and the capacitor is initially discharged, find the output voltage at time just before $t = 3\text{ ms}$. (Hint, make a sketch of the output waveform).



$$v_o \Big|_{t = 3\text{ ms}} =$$

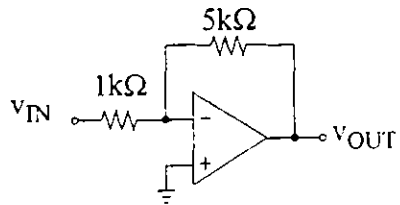[5] **Question 2:** The opamp in the circuit below is ideal except for a unity-gain bandwidth of $\omega_t = 2 \times 10^7$ rad/sec and a slew-rate of $SR \approx 1$ V/ μ sec. Given that the input will be a step function, find the maximum size of the input step before the opamp slew-rate limits




Max input step =

[5] **Question 3:** A given diode is measured to have an on voltage of 0.65V when a current of 1mA is applied through it. In addition, it is found that for every decade increase in current, the diode on voltage increases by 0.11V. Find n and I_s for this diode. ($V_T = 25\text{mV}$)


 $n =$ $I_s =$

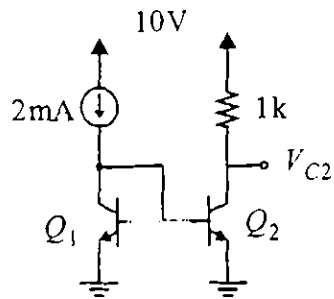[5] Question 4: Assuming $\beta = 20$ and $I_{s2} = 2I_{s1}$, find the voltage, V_{C2} . Ignore the Early effect.



$V_{C2} =$

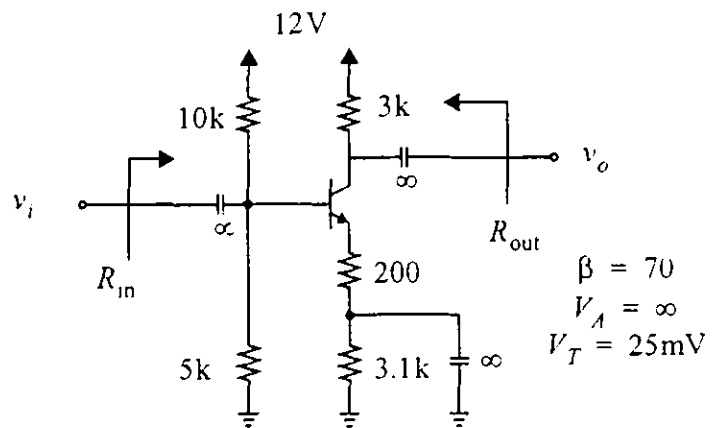[5] **Question 5:** For the circuit below find the small-signal gain v_o/v_i , input resistance R_{in} and output resistance R_{out} . For dc analysis assume β goes to infinity.




$$\frac{v_o}{v_i} =$$

$$R_{in} =$$

$$R_{out} =$$

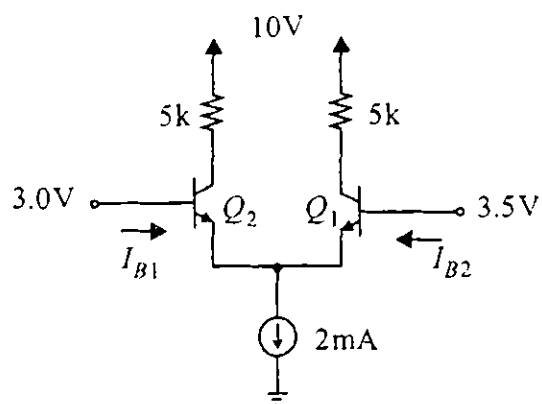
[5] **Question 6:** For the circuit below, find the base currents, I_{B1} and I_{B2} . For the transistors, $\beta = 100$, $V_A = \infty$, and $V_{CESAT} = 0.2V$.



$I_{B1} =$

$I_{B2} =$

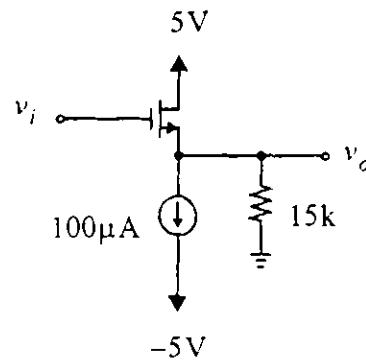
[5] **Question 7:** An NMOS transistor with $W = 10\mu\text{m}$ and $L = 0.5\mu\text{m}$ in a technology with $\mu_n C_{ox} = 100\mu\text{A/V}^2$ and $V_t = 1\text{V}$ is used in the circuit below. Ignoring the Early effect, find v_o/v_i when the dc value of v_i is adjusted such that v_o is biased to zero volts. Also find the minimum output voltage.



$$\frac{v_o}{v_i} =$$

$$v_o|_{\min} =$$

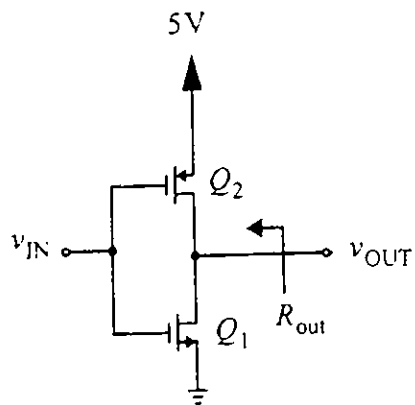[5] Question 8: For the CMOS inverter shown below, find the output resistance when $v_{IN} = 0V$.




$$\mu_n C_{ox} = 3\mu_p C_{ox} = 100 \mu A/V^2$$

$$V_{tn} = |V_{tp}| = 1V$$

$$\left(\frac{W}{L}\right)_1 = 10 \quad \left(\frac{W}{L}\right)_2 = 20$$

$R_{out} =$

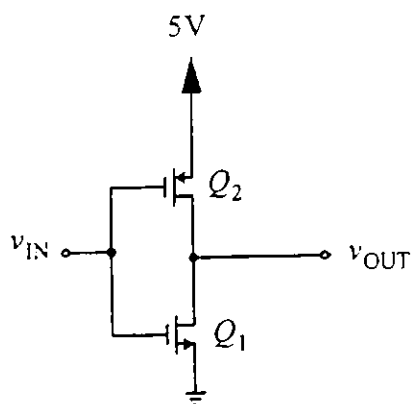[5] **Question 9:** For the CMOS inverter shown below, find the size of Q_2 such that when the Early effect is ignored, the small-signal gain goes to minus infinity at $v_{IN} = 2.0\text{V}$.




$$\mu_n C_{ox} = 3\mu_p C_{ox} = 100\mu\text{A/V}^2$$

$$V_{tn} = |V_{tp}| = 1\text{V}$$

$$\left(\frac{W}{L}\right)_1 = 10$$

$\left(\frac{W}{L}\right)_2 =$

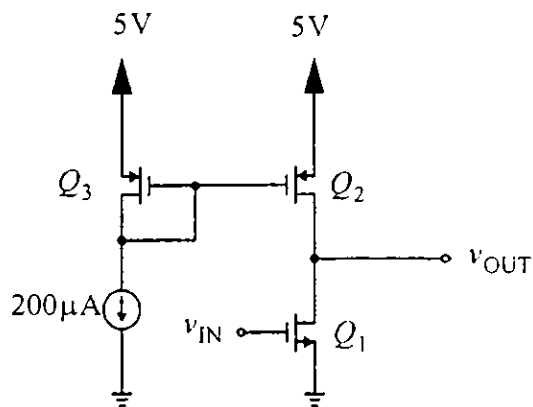[5] **Question 10:** Consider the circuit below. Given that the output voltage is equal to $v_{OUT} = 4.9V$, find the current, I_{D2} . Ignore the finite-output impedance of the transistors.



$$\mu_n C_{ox} = 3\mu_p C_{ox} = 100\mu A/V^2$$

$$V_{in} = |V_{tp}| = 1V$$

$$\left(\frac{W}{L}\right)_1 = 10 \quad \left(\frac{W}{L}\right)_2 = 10 \quad \left(\frac{W}{L}\right)_3 = 20$$

$$I_{D2} =$$

Last Name: _____

Scratch sheet (can be used for rough calculations)