

University of Toronto
Faculty of Applied Science and Engineering
Final Examination, April 16, 2001
Fourth Year-Program: Mechanical and Industrial Engineering
MIE 438S: Microprocessors Applications
Examination Type: A
Examiners - Andrew A. Goldenberg and William W. Melek

QUESTION 1

(20%)

Given the diagram in Figure 1,

- (i) Identify what tasks could this unit perform.
- (ii) For each task identified in (i), what is the state of each switch (S_1 , S_2 , S_3 , and S_4).

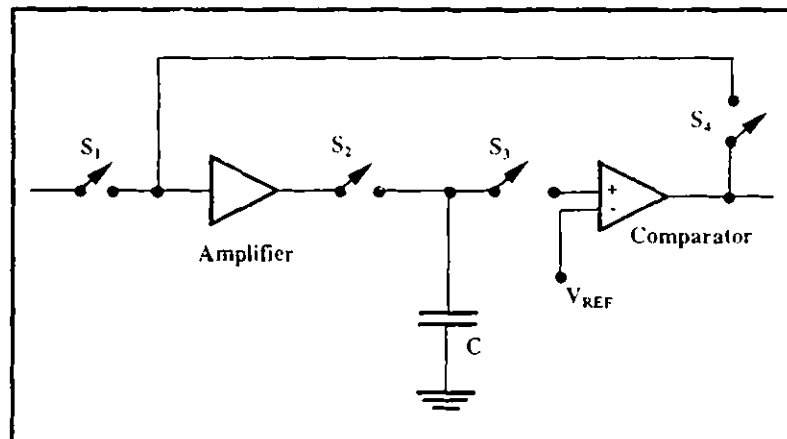


Figure 1

QUESTION 2

(23%)

(a) Define the following terms:

1. Stepper motor slew range.
2. Software Latency.
3. Pipelining of the CPU instructions.

-

2.

$$\frac{1}{2}$$


二

-

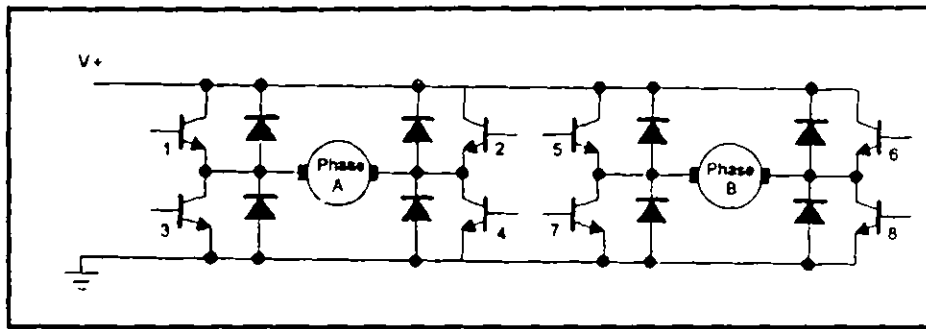


Figure 3

Question 5

(15%)

Identify the gate shown in Figure 4. Explain the logic that the identified gate implements.

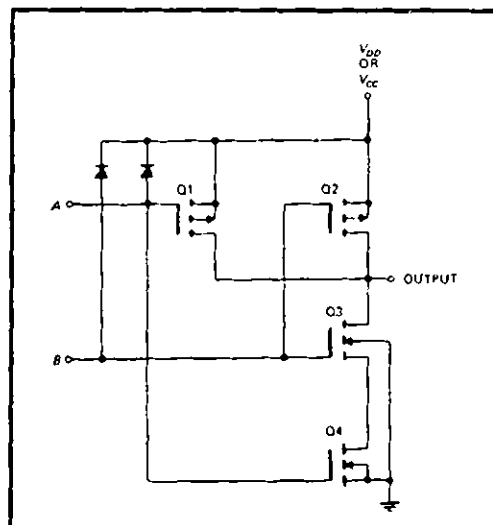


Figure 4