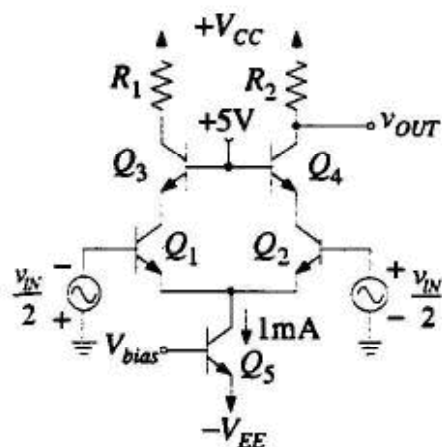


QUESTION (1)

In the following circuits, assume that $\beta = 100$, $V_{BE} = 0.7\text{V}$, $V_{CE(sat)} = 0.4\text{V}$ and $V_A = 100\text{V}$ for all transistors.



Given:

$$R_1 = R_2 = 10\text{k}\Omega$$

$$V_{CC} = V_{EE} = 10\text{V}$$


$$V_{bias} \text{ is adjusted such that } I_{C5} = 1\text{mA}$$

$$V_T = 25\text{mV}$$

- Estimate the differential gain v_{OUT}/v_{IN} in (V/V). (4 points)
- Find the differential input resistance R_{id} . (2 points)
- Find the common mode input resistance R_{icm} . (4 points)
- Find the common mode input range. (4 points)
- Estimate the common mode rejection ratio, CMRR. Express your result in dB. (6 points)

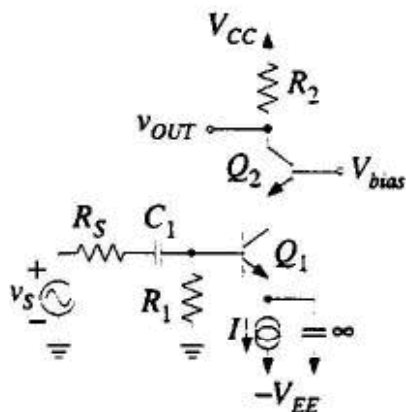QUESTION (2)

In the following circuit, assume that $\beta = 100$, $V_{BE} = 0.7\text{V}$, $V_{CE(sat)} = 0.4\text{V}$, $V_A = 100\text{V}$, $C_\mu = 2\text{pF}$ for all transistors. Neglect r_x and r_O .



Given:

$$R_1 = 100\text{k}\Omega$$

$$R_2 = 5\text{k}\Omega$$

$$R_S = 600\Omega$$

$$C_1 = 1\mu\text{F}$$

$$I = 1\text{mA}$$

$$V_{CC} = V_{EE} = 10\text{V}$$


$$V_{bias} = 5\text{V}$$

$$V_T = 25\text{mV}$$

- Estimate the mid-band gain v_{OUT}/v_S in (V/V). (4 points)
- Find the lower 3dB frequency f_L in (Hz). (4 points)
- Find the upper 3dB frequency f_H in (Hz). (6 points)
- Find the 2nd high frequency dominant pole in (Hz). (6 points)

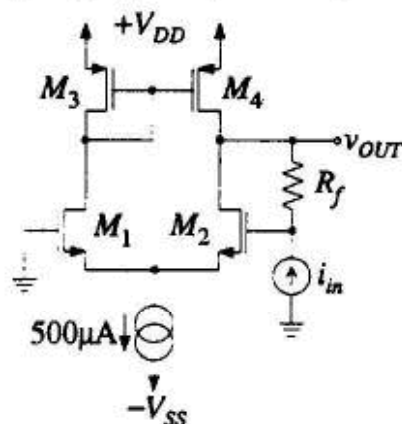QUESTION (3)

The following CMOS trans-resistance amplifier have a feedback resistor R_f . Assume that all n -MOSFETs have $k'_n = \mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_{tn} = 1\text{V}$, and $\lambda_n = V_{An}^{-1} = 0.02\text{V}^{-1}$. All p -MOSFETs have $k'_p = \mu_p C_{ox} = 25 \mu\text{A}/\text{V}^2$, $V_{tp} = -1\text{V}$, and $\lambda_p = V_{Ap}^{-1} = 0.02\text{V}^{-1}$.



Given:

M_1 and M_2 has $(W/L)_{1,2} = 120\mu\text{m}/3\mu\text{m}$


M_3 and M_4 has $(W/L)_{3,4} = 60\mu\text{m}/3\mu\text{m}$

$R_f = 100\text{k}\Omega$,

- Find the closed loop trans-resistance gain v_{OUT}/i_{in} in (V/A) (12 points)
- Find the input resistance, R_{if} seen by the input current source i_{in} . (4 points)
- Find the output resistance, R_{of} at the output terminal. (4 points)

QUESTION (4)

The following class AB amplifier stage is biased such that the dc output voltage is 0V if the input voltage, v_S is zero. The forward voltage drop of the diodes D_1 and D_2 are 0.7V and the $|V_{BE}|$ for the complementary power transistors Q_1 and Q_2 are 0.6V (independent of current level). The input voltage, v_S is supplied by an ideal voltage amplifier.

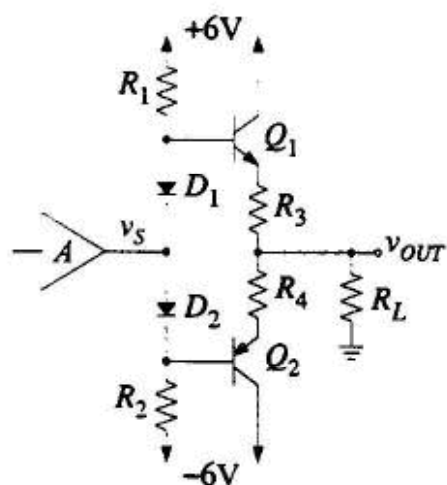

Given:

$\beta = 50$ for Q_1 and Q_2

$|V_{CE(sat)}| = 0.3\text{V}$ for Q_1 and Q_2

$R_1 = R_2 = 560\Omega$


$R_3 = R_4 = 10\Omega$

$R_L = 8\Omega$,

- Estimate the standby power, $P_{standby}$ with $v_S = 0\text{V}$ (not including the amplifier A) (6 points)
- Find the maximum peak to peak output voltage swing, $V_{O(p-p)}$ (4 points)
- Find the maximum rms output power, $P_{out(max)}$ that can be delivered to R_L (4 points)
- Find the efficiency, η of this output stage when delivering maximum output power (6 points)

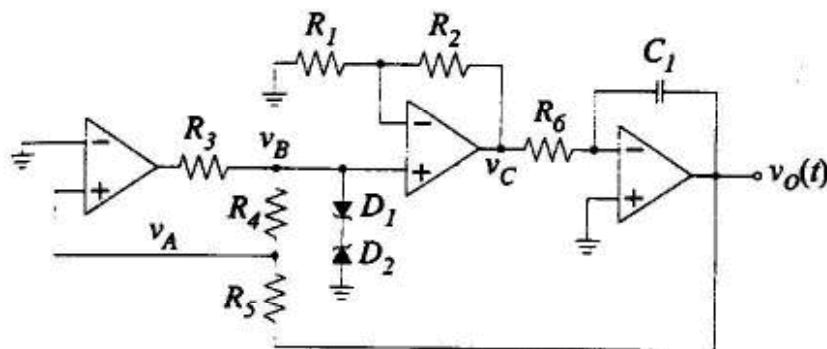QUESTION (5)

In the following circuit, assume that all op amps are ideal, the zener diodes have a forward voltage drop of 0.7V and V_Z of 6.8V and $r_Z = 0\Omega$. $V_Z = 6.8V$. Assume that the circuit has reached steady state operation.



Given:

$$R_1 = R_4 = R_6 = 10k\Omega$$

$$R_2 = 6k\Omega$$

$$R_3 = 1k\Omega,$$

$$R_5 = 20k\Omega,$$

$$C_1 = 0.1\mu F$$

- Find the peak to peak voltage swing at v_B . (4 points)
- Find the peak to peak voltage swing at $v_o(t)$. (6 points)
- Find the oscillation frequency of $v_o(t)$ in (Hz). (6 points)
- Sketch the waveforms of v_B and $v_o(t)$ on a set of common voltage-time axes. (4 points)