
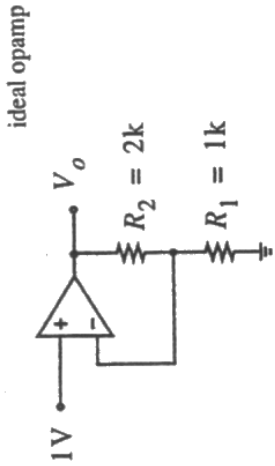


[5] Question 2:

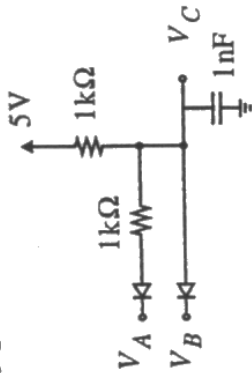


For the above circuit, find the output voltage,  $V_o$

[5] Question 3:




Use the 0.7V constant voltage drop model for the diodes.

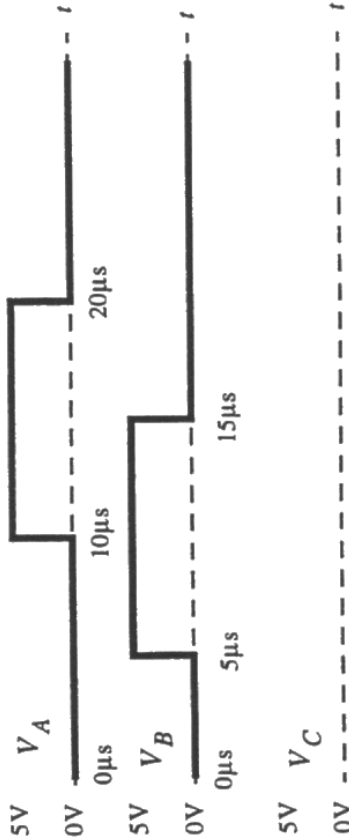Sketch the resulting waveform for  $V_C$  on the graph below and label important voltages and important time constants.




[5] Question 4:

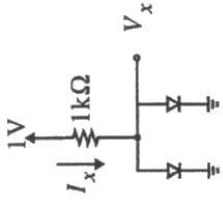

Use the exponential model for the diodes.


Consider the circuit above where the two diodes are identical. Given that each diode would have a current of 2mA at a voltage of 0.7V and that its voltage drop changes by 0.1V for every decade change in current, find the current,  $I_x$  and the voltage,  $V_x$ .

[5] Question 5:

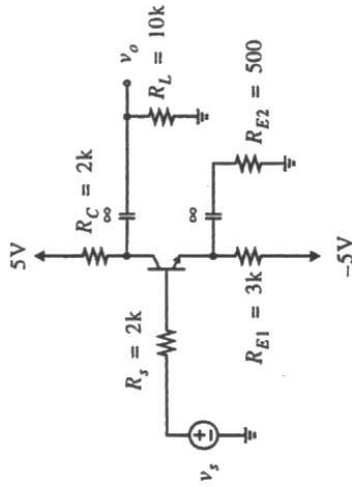


For the above transistor circuit, find the values of the collector current, base voltage, collector voltage and emitter voltage. Assume  $\beta = 100$  and ignore any finite output resistance.

[5] Question 6:

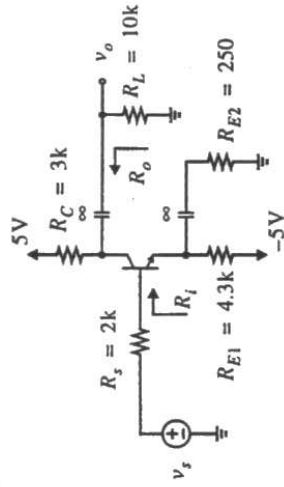


For the above transistor circuit, the collector current was found to be 1mA and the transistor is operating in the active region. Using small-signal analysis, find the gain,  $v_o/v_i$ , input resistance,  $R_i$  and output resistance,  $R_o$ . Assume  $\beta = 100$  and ignore any finite output resistance.

[5] Question 7:

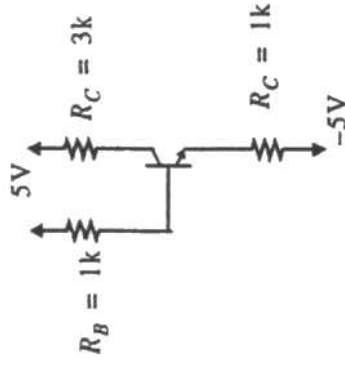


For the above circuit, find  $V_B$ ,  $V_C$  and  $V_E$ . Assume  $\beta = 100$  and ignore finite output resistance.

[5] Question 8:

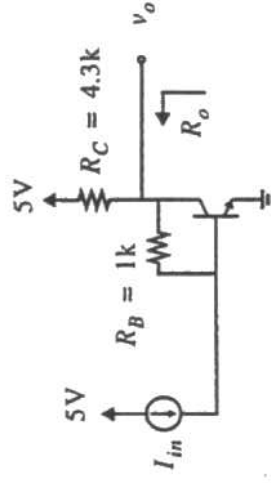

The above is a transimpedance amplifier (used in photodetectors). Find the output resistance,  $R_o$ . Assume  $\beta = 100$  and ignore finite output resistance.

[5] Question 9:

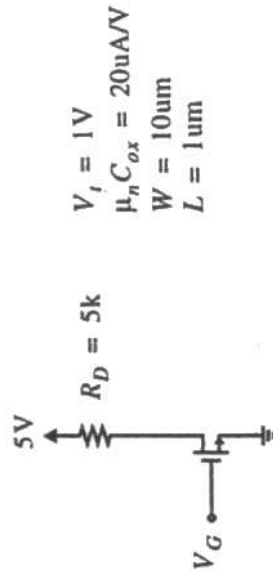

For the above circuit, find the value of  $V_G$  where the transistor is at the edge of the triode region.