

UNIVERSITY OF TORONTO  
Faculty of Applied Science and Engineering  
FINAL EXAM

MIE346S Analog and Digital Electronics for Mechatronics

Examiner: Omid S. Jahromi


Test time: 2 hours and 30 minutes

Test Type: D

This test has 5 pages including the cover page.


April 17th, 2001

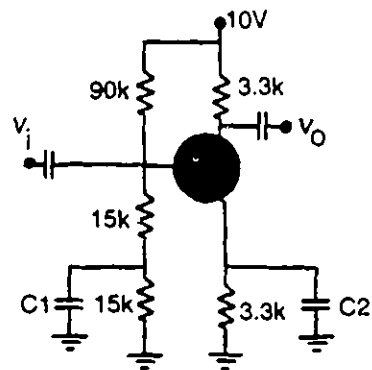**Problem 1 (25 marks):** A Silicon NPN transistor with  $\beta = h_{fe} = 50$  is used to build an amplifier as shown in the circuit below.



- (a) Find the DC voltages at the base, collector and emitter.
- (b) Calculate the output voltage  $v_o(t)$  if  $v_i(t) = 0.01 \sin(2\pi \times 10^6 t)$  volts. (All the capacitors can be assumed short-circuit at input signal's frequency.)
- (c) Explain in words how  $v_o(t)$  might change if
  - i. the capacitor  $C_1$  is removed,
  - ii. the capacitor  $C_2$  is removed.

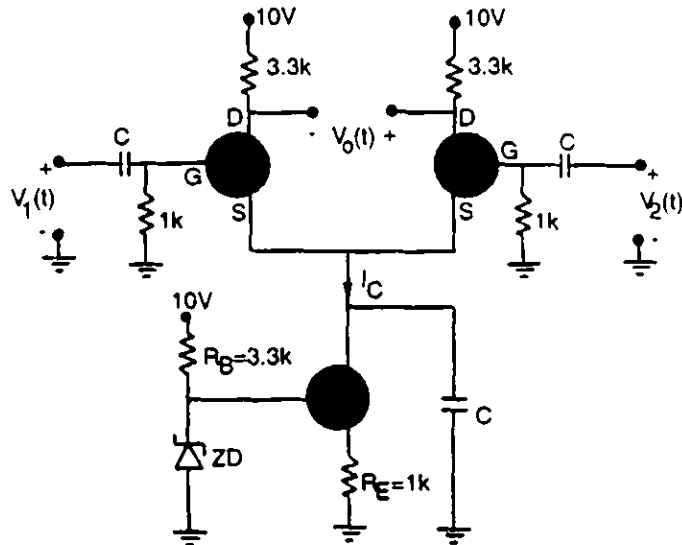**Problem 2 (30 marks):** The circuit below shows a differential amplifier designed using two identical FETs and a BJT. The FETs used have  $I_{DSS} = 9\text{mA}$  and  $V_P = -6\text{V}$ . The BJT is made of Silicon and has  $\beta = 50$ . The Zener diode  $ZD$  operates at a break-down voltage of  $2.7\text{V}$ .




- The BJT serves as a current source. Calculate the current  $I_C$  provided by it.
- Now, let  $V_1(t) = 0.01 \cos(2\pi \times 10^3 t)$  and  $V_2(t) = -V_1(t)$  be the input signals. Calculate  $V_o(t)$  using an appropriate small-signal model. (All the capacitors might be assumed short-circuit at the input signals' frequency.)
- Explain in words how  $v_o(t)$  might change if
  - $R_B$  is decreased,
  - $R_E$  is decreased.

**Problem 3 (25 marks):** A small-signal amplifier (shown below) is used by a student to measure the common-base hybrid-h parameters of an unknown transistor. She assembles the circuit in the lab and chooses  $R_1$  and  $R_2$  to make sure that the transistor is biased in its active region.

She also sets a signal generator to generate a  $10\text{KHz}$  sinusoidal signal and connects it to the circuit's input. She then makes the following AC (small-signal) measurements:

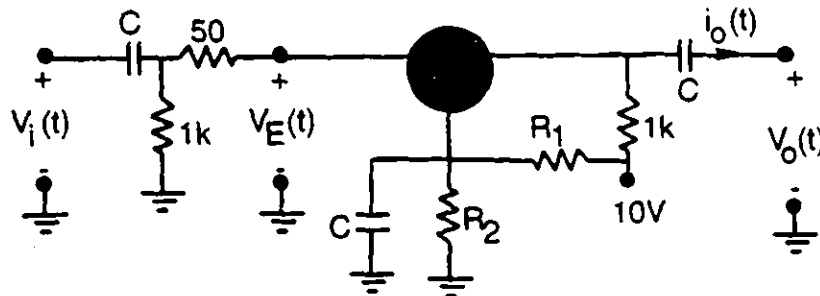- (1.)  $v_i = 100\text{mV}$  peak-to-peak,
- (2.)  $v_e = 50\text{mV}$  peak-to-peak,
- (3.)  $v_o = 1\text{V}$  peak-to-peak when output is open-circuit,
- (4.)  $i_o = 2\text{mA}$  peak-to-peak when output is short-circuit.



- (a) Draw the small-signal equivalent circuit for this amplifier. Assume that all the capacitors are short-circuit at input signal's frequency.
- (b) Use the measurements made by this student to calculate the numerical values of  $h_{ib}$ ,  $h_{fb}$  and  $h_{ob}$ . Assume that  $h_{rb} = 0$  for simplicity.

**Problem 4 (20 marks):** Consider the circuit shown below. The BJTs are made of Silicon and have  $\beta = 5$ . The MOSFET is an "enhancement" type. It is known that  $V_o = 1V$  when point  $X$  is connected to point  $C$  and that  $V_o = 9V$  when point  $X$  is connected to point  $B$ . Find  $V_o$  when point  $X$  is connected to point  $A$ .

