

UNIVERSITY OF TORONTO  
FACULTY OF APPLIED SCIENCE AND ENGINEERING

FINAL EXAMINATION  
APRIL 2000  
EXAM TYPE: A  
First Year Programs: 01, 02, 03, 04, 06, 08

Q1	/25
Q2	/25
Q3	/25
Q4	/25
Total	/100

ECE 110S: ELECTRICAL FUNDAMENTALS

EXAMINERS: N.P. Kherani, L. de Windt, B. Wang, S. Zukotynski (*Co-ordinator*)

NAME: \_\_\_\_\_  
Last First

STUDENT NO.: \_\_\_\_\_

INSTRUCTIONS:

- This is a Type A examination; no aids are allowed.
- Only non-programmable calculators are allowed (the allowed models are specified in the Faculty Calendar).
- Answer all parts of all four questions.
- All four questions are of equal weight.
- The weight of each of the individual parts of each question is stated in the margins.
- All work is to be done on these pages.
- Place your final answers in the provided boxes unless instructed otherwise.
- When answering the questions include all the steps of your work on these pages. For additional space, you may use the back of the preceding page.
- Do not unstaple this exam.

CONSTANTS:

$e = 1.6 \times 10^{-19} \text{C}$        $\epsilon_0 = 8.85 \times 10^{-12} \text{F/m}$        $\mu_0 = 4 \times 10^{-7} \text{H/m}$

**Question 1: Electricity and Magnetism****PART A: General**


Complete the following sentences:

- [1] (i) Electrostatics is a study of \_\_\_\_\_ .
- [1] (ii) Electrical and Magnetic phenomena stem from a property of matter known as \_\_\_\_\_ .
- [1] (iii) Materials in which charges cannot move are known as \_\_\_\_\_ or \_\_\_\_\_ .
- [1] (iv) The work  $W$  done by a charge  $Q$  as it (the charge) lowers its potential by  $V$  is mathematically expressed as \_\_\_\_\_ .
- [1] (v) A solenoid in its simplest form is \_\_\_\_\_ .

Question 1: Electricity and Magnetism

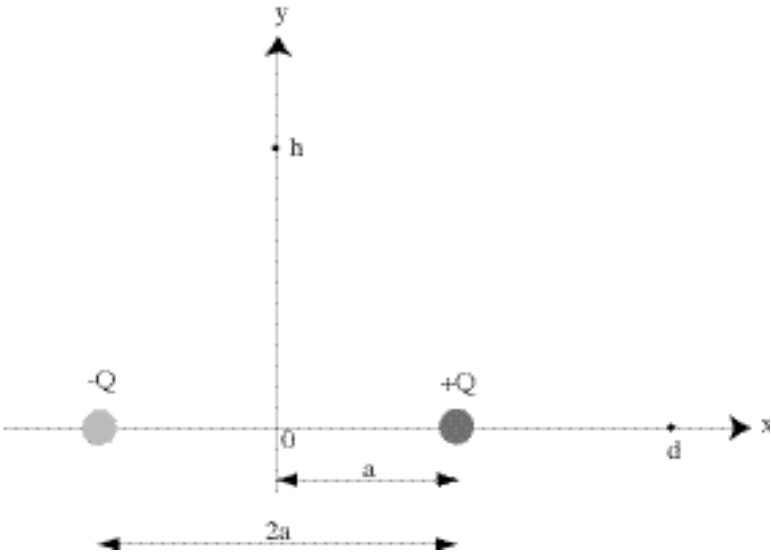PART B: Electric Field and Electric Potential

Consider the electric dipole shown in the figure below.



- [4] (i) Determine the electric field, including its direction, at  $x = d$ , where  $d > a$ , due to the given electric dipole.

**E** =

- [2] (ii) A positive point charge  $q$  is placed at  $x = d$ . Determine the electric force, including its direction, experienced by the test charge due to the given dipole.

**F** =

- [1] (iii) Draw several electric field lines for the given dipole on the above figure.


- [2] (iv) If the electric potential at the origin is 0, determine the electric potential at  $y = h$ . Explain your result.

$V(x=0, y=h) =$

### Question 1: Electricity and Magnetism
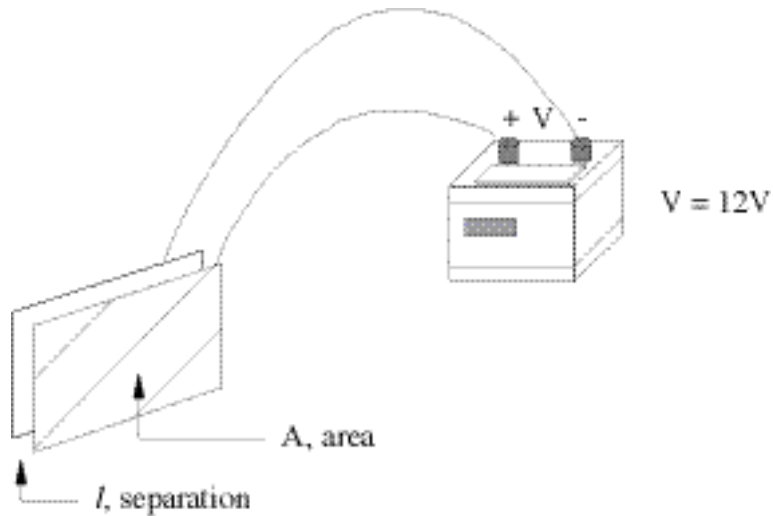
#### PART C: Capacitors

A 12 V battery is connected to the parallel plates as shown in the figure below.



- [2] (i) If the positively charged parallel plate has an electrical charge of 12 nC and the negatively charged plate -12 nC, compute the capacitance  $C$  for the given parallel plate capacitor.

$C =$

- [2] (ii) If the spacing between the parallel plates is  $l = 0.001$  m, compute the area  $A$  of the parallel plates.

$A =$

- [1] (iii) Potential difference is generally expressed as  $V_f - V_i = - \int_i^f \mathbf{E} \cdot d\mathbf{r}$ .


Using this expression, compute the strength of the electric field between the charged parallel plates.

$|\mathbf{E}| =$

**Question 1: Electricity and Magnetism**

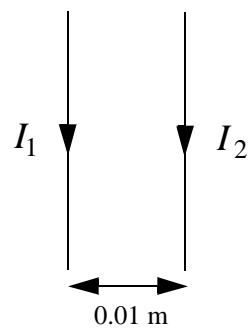**PART D:** Magnetic Field and Magnetic Force

Two long, parallel conductors separated by a distance of 0.10 m carry currents in the same direction. The first conductor carries a current  $I_1 = 10A$  and the second conductor carries current  $I_2 = 8A$ .



- [3] (i) Calculate the magnetic field at conductor 2 due to the current  $I_1$  in conductor 1.


$ \mathbf{B}  =$
Direction:

- [3] (ii) Calculate the magnetic force per unit length exerted on  $I_2$  by  $I_1$ .

$ \mathbf{F}  =$
Direction:

### Question 2: DC Circuits

Consider the circuit shown below.

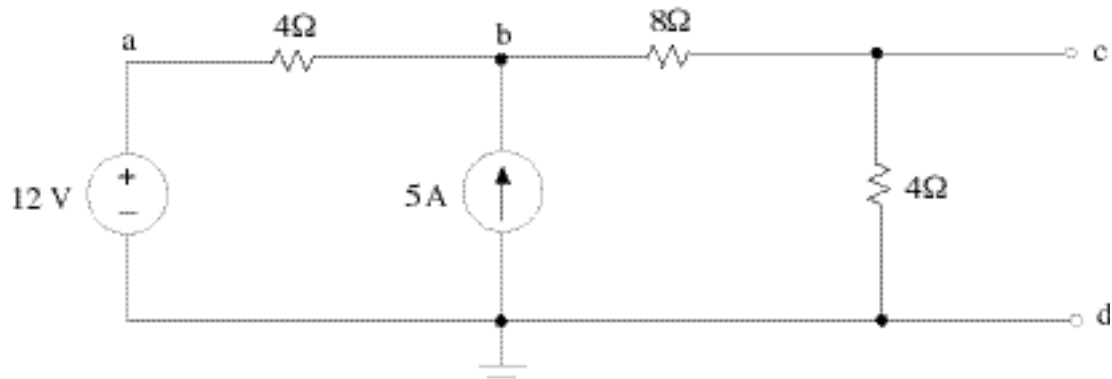

- [4] (i) Use Nodal Analysis to find the voltage  $V_b$ .

$V_b =$

- [2] (ii) Determine the voltage  $V_{cd}$ .

$V_{cd} =$

- [4] (iii) Find the total power supplied by the sources.

$P_s =$

**Question 2: DC Circuits**

- [7] (iv) Use the Principle of Superposition to determine the voltage  $V_{cd}$ .

$$V'_{cd} \text{ (due to 12 V) =}$$

$$V''_{cd} \text{ (due to 5 A) =}$$

$$V_{cd} =$$

- [3] (v) Determine the equivalent resistance seen between terminals c and d.

$$R_{eq} =$$


- [5] (vi) Determine the Norton equivalent circuit with respect to terminals c and d.

$$I_N =$$

$$R_N =$$

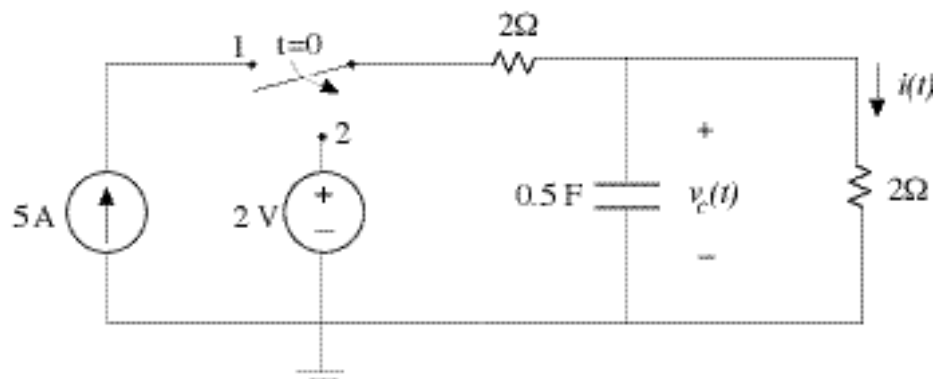Question 3: Transient Analysis

For the circuit shown below, assume that the switch stayed at position 1 for a long time and that it changed from position 1 to position 2 at time  $t = 0$ .



[4] (i) Find  $v_c(t)$  for  $t = 0^-$  and  $t = 0^+$ .

$v_c(0^-) =$

$v_c(0^+) =$

[10] (ii) Derive the differential equation in  $v_c(t)$  for  $t > 0$ .

Differential equation  $v_c(t)$  for  $t > 0$ :




Question 3: Transient Analysis

[6] (iii) Find  $v_c(t)$  and  $i(t)$  as functions of time for  $t > 0$ .

$v_c(t)$  for  $t>0$ :

$i(t)$  for  $t>0$ :

[5] (iv) Sketch  $v_c(t)$  for all time; clearly label the axes.

 

**Question 4: AC Circuits**

A 10 MHz sinusoidal wave generator has an open circuit voltage of 0.5 V (peak voltage) in magnitude. The output (Thévenin) impedance of the generator consists of a 50  $\Omega$  resistor connected in parallel to a 100 pF capacitor.

A load, which is attached to the output terminals of the generator, consists of a 100  $\Omega$  resistor connected in parallel to a 50 pF capacitor.

- [5] (i) Draw a schematic diagram of the circuit in the time domain; include the value of all the components.

Time domain

Frequency domain

**Question 4: AC Circuits**

[4] (iii) Determine the current in the load. State the value of the current in the frequency domain.

Frequency domain

[4] (iv) Give the value of the current in the load in the time domain.

Time domain

[3] (v) Give the value of the voltage across the load in the frequency domain.

Frequency domain

[4] (vi) Determine the power delivered to the load. Specifically, give the Apparent power, Real power, Reactive power and the Power Factor (PF).

Apparent power

Real power

Reactive power

Power Factor (PF)